

**Code:**

```
module oneBit_AddSub(res,cout,sbit,a,b,c);
```

```
output reg res,cout;
```

```
input sbit,a,b,c;
```

always@(a,b,c,sbit)begin

```
case(sbit)
```

```
1'b0:begin
```

```
res = a^b^c;
```

```
cout << (a&b)|(c&b)|(a&c);
```

end

```
1'b1:begin
```

```
res = a^b^c;
```

```
cout = (~a & b) | (b & c) | (~& a);
```


end

endcase

end

endmodule

Output;

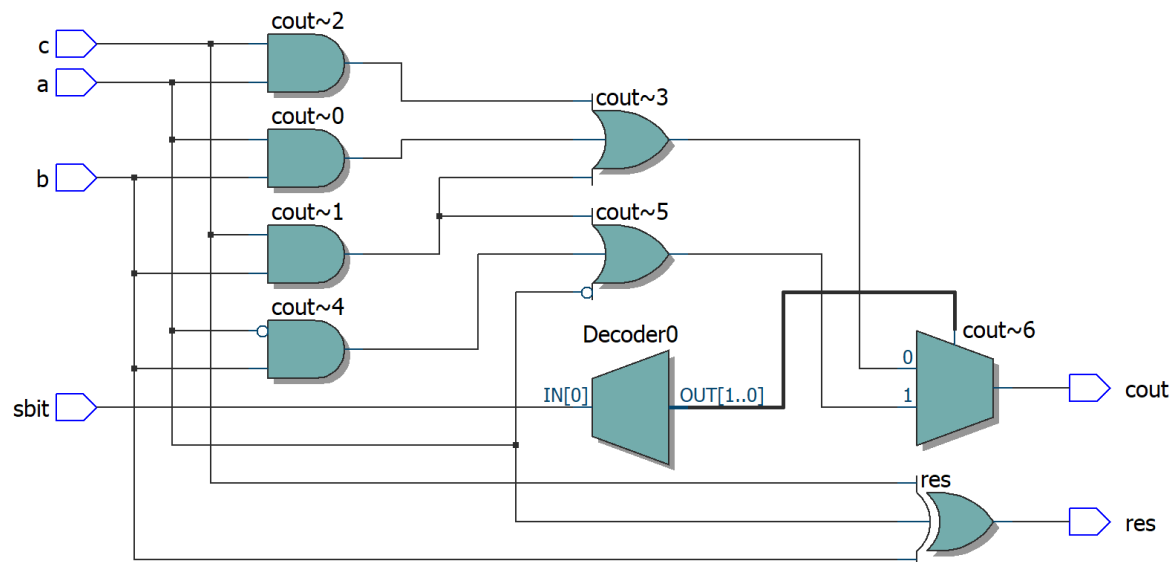

**Subtraction:**

Instruction					
/oneBit_AddSub/res	0				
/oneBit_AddSub/cout	0				
/oneBit_AddSub/sbit	St1				
/oneBit_AddSub/a	St1				
/oneBit_AddSub/b	St1				
/oneBit_AddSub/c	St0				

**Addition:**

[illegible]

2) 16 bit full adder.

```
module fulladder #(parameter N = 16)(
  input wire [N-1:0] a,
  input wire [N-1:0] b,
  input wire c_in,
  output wire [N-1:0] sum,
  output wire c_out
);

  wire [N:0]temp;
  wire [N-1:0]c_next;

  assign temp[0] = c_in;

  genvar i;
  generate
    for (i = 0; i < 16; i = i+1) begin : bit_adder
      full_adder fa (
        .a(a[i]),
        .b(b[i]),
        .c_in(temp[i]),
        .sum(sum[i]),
        .c_out(c_next[i])
      );
      assign temp[i+1] = c_next[i];
    end
  endgenerate
  assign c_out = c_next[N-1];
endmodule


module full_adder (
  input wire a,
  input wire b,
  input wire c_in,
  output wire sum,
  output wire c_out
);
  assign sum = a ^ b ^ c_in;
  assign c_out = (a & b) | (c_in & (a ^ b));
endmodule
```

Output

Simulation Results:

+ /fulladder/a	3927	2						3927	
+ /fulladder/b	10	3			10				
+ /fulladder/c_in	St0								
+ /fulladder/sum	3937	5			12			3937	
+ /fulladder/c_out	St0								

RTL View:

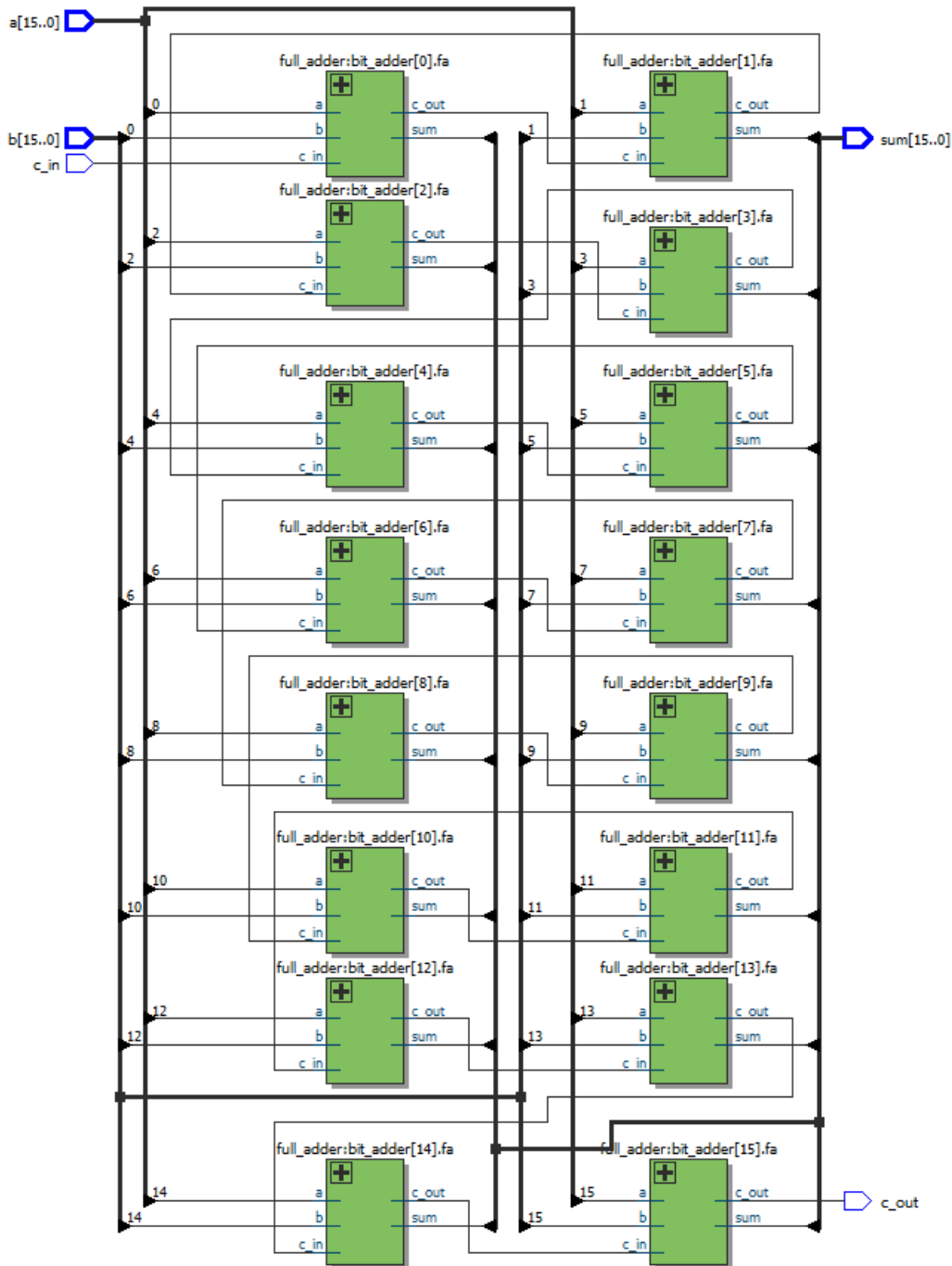

### 3) 16 bit adder subtractor.

#### Code:

```
module subAdder #(parameter N = 16)(a,b,c_in,sum,c_out);

input [N-1:0]a,b;
input c_in;


output reg [N-1:0]sum;
output reg c_out;

reg [N-1:0] Btemp;


always@(*)begin
    if(c_in)begin
        Btemp = ~b;
    end
    else Btemp = b;
    {c_out,sum} = a + Btemp + c_in;
end

endmodule
```

#### Simulation:

 

#### RTL View:

 

### 4) Look ahead carry adder

#### Code:

```
module lookAheadCarryAdder #(parameter N = 16)(input [N-1:0]a,b,
    input c_in,
    output [N-1:0] sum,
    output c_out);

wire [N:0]C;
wire [N-1:0] G,P,SUM;

assign C[0] = c_in;

genvar i;
generate
    for(i = 0; i < N; i = i+1)begin:ll
        adder a1(.a(a[i]),.b(b[i]),.c(C[i]),.sum(SUM[i]),.cout());
    end
endgenerate

genvar j;
generate
```

```

for(j = 0; j < N; j = j+1)begin:l2
    assign G[j] = a[j] & b[j];
    assign P[j] = a[j] ^ b[j];
    assign C[j+1] = G[j] | (P[j]&C[j]);
end
endgenerate

```

```

assign sum = SUM;
assign c_out = C[N];

endmodule

```

```


module adder(input a,b,c,
             output reg sum,cout);

always@(*)begin
    {cout,sum} = a+b+c;
end






endmodule
 
```

### RTL View:



### Simutlation:

	/lookAheadCarryAdder/a	245	245	
	/lookAheadCarryAdder/b	119	119	
	/lookAheadCarryAdder/c_in	St1		
	/lookAheadCarryAdder/sum	365	364	365
	/lookAheadCarryAdder/c_out	St0		