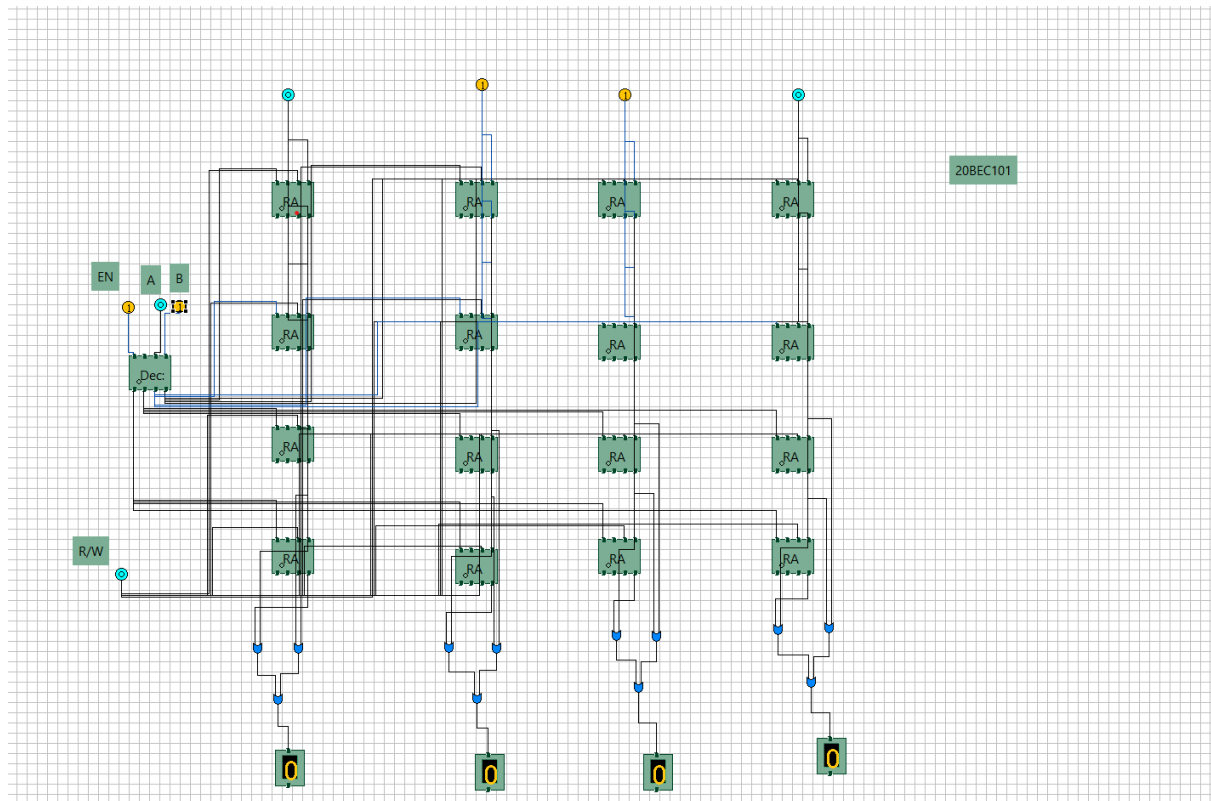



# COMPUTER ARCHITECTURE

## COAS RAM

Write:



Read:

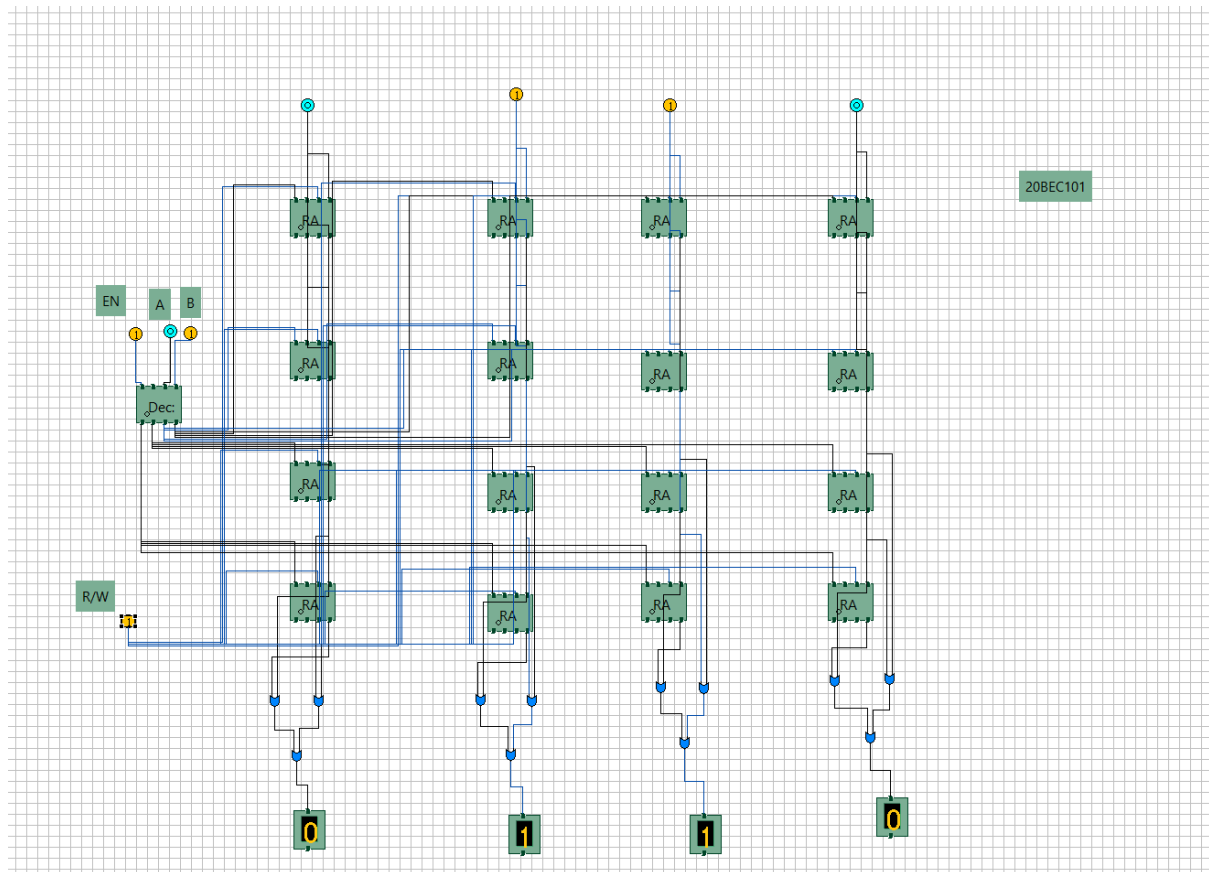

#### Q4) Write 4x8 RAM using Verilog HDL

**Code:**

```
module ram4x8(
    input [1:0] addrLine,
    input r_wBar,clk,
    input [7:0] write,
    output reg [7:0] read
);
```

```
reg [7:0] mem [3:0];
```

```
always@(posedge clk)begin
```

```
    if(r_wBar)begin
```

```
        read <= mem[addrLine];
```

```

        end

        else begin

            mem[addrLine] <= write;

        end


    end

end

Endmodule


```

**RTL:**

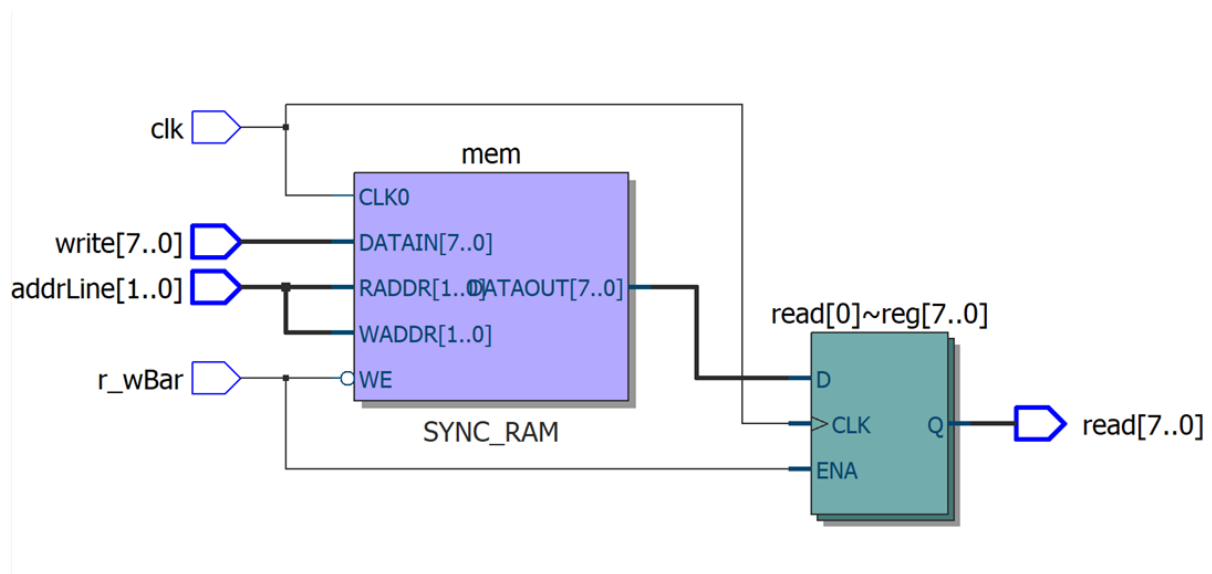


**Simulation:**

**Write:**

 

**Read:**

 

**Q5) Write a Verilog code for 4X8 PROM and perform the functional simulation.**

**Code:**

```
module prom4x8(
    input [1:0] addrLine,
    input clk,read,
    output reg [7:0] out
);


reg [7:0] prom [3:0];

initial begin
    prom[0] = 12;
    prom[1] = 13;
    prom[2] = 14;
    prom[3] = 15;
end


always@(posedge clk)begin
    if(read) begin
        out <= prom[addrLine];
    end
end

endmodule
```

**RTL:**

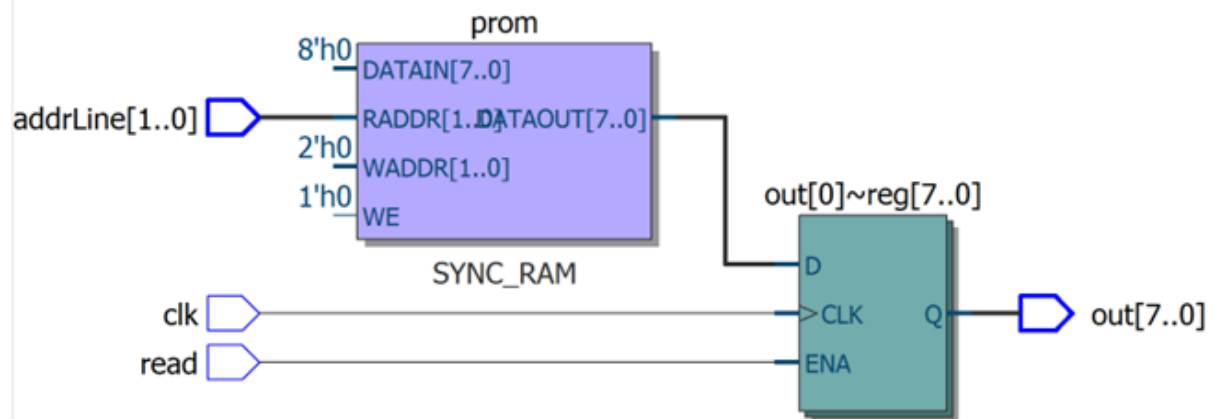

### Simulation:

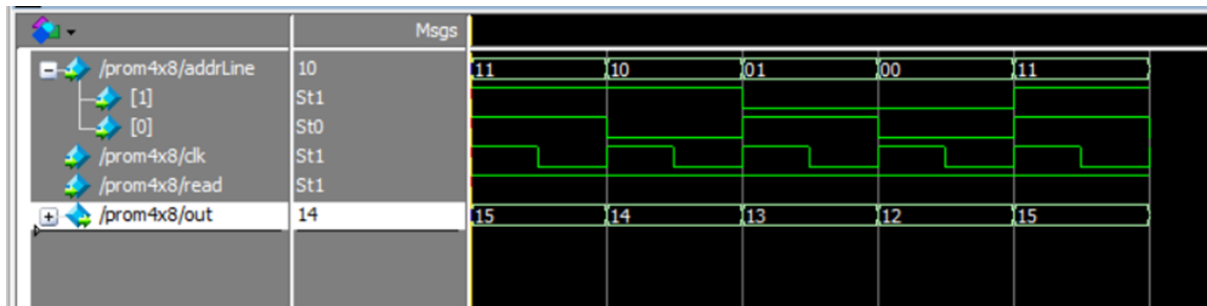

### Q.6) dual RAM

#### Code:

```

module dualPortRam #(parameter N = 32,
                      parameter Add = $clog2(N),
                      parameter B = 8)(
    input [B-1:0]dataIn,
    input  wr,clk,
    input [Add-1:0] addrLine1,addrLine2,
    output [B-1:0] dataOut1, dataOut2
);

reg [B-1:0] mem [N-1:0];

```

```

integer i;

initial begin
    for(i=0; i < N; i=i+1)begin
        mem[i] <= i+1;
    end
end


always @ (posedge clk)begin
    if(wr)begin
        mem[addrLine1] <= dataIn;
    end
end

assign dataOut1 = mem[addrLine1];
assign dataOut2 = mem[addrLine2];

endmodule

```

## RTL:

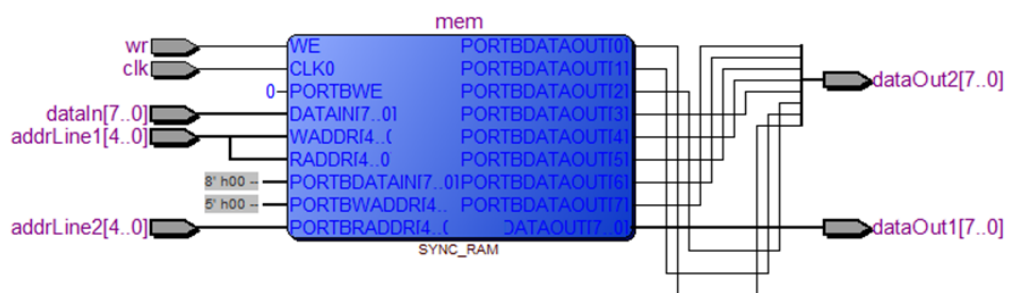

## Simulation:

